

## CS 2104-01 Hardware Lab

Lab 10 May 5, 2015

### Digital Lock

**Lab report** (upload to iLMS before 5/12 3:30p.m.)

Your report should include the following:


- description and explanation of your work (including answers to all questions in the pre-lab)

藉由前幾次學過的 keypad scanner 以及 buzzer，結合 14 segment display 的控制，即可做出此次的密碼鎖，我直接在 keypad\_scanner.v 裏頭修改按下按鍵後的反應，藉此控制密碼的顯示和是否啟動警鈴，或者讓它回到最初始化的狀態。


**Pre-lab** (Finish it before coming to the class)

Prepare the following before class so you may complete this lab smoothly.

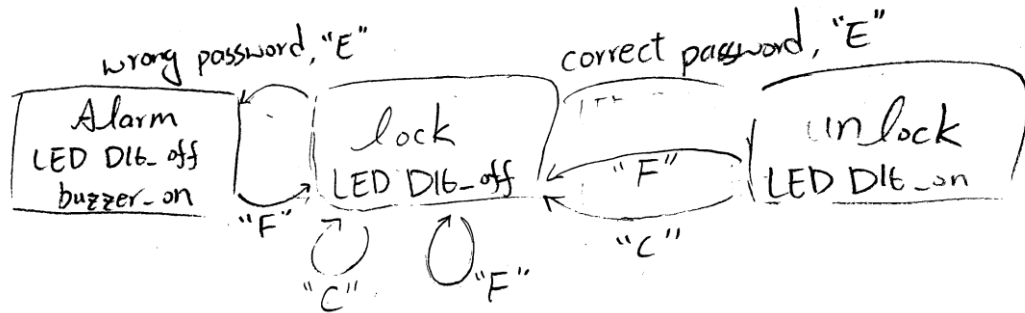- Draw a state transition diagram or algorithmic state machine chart for the digital lock.



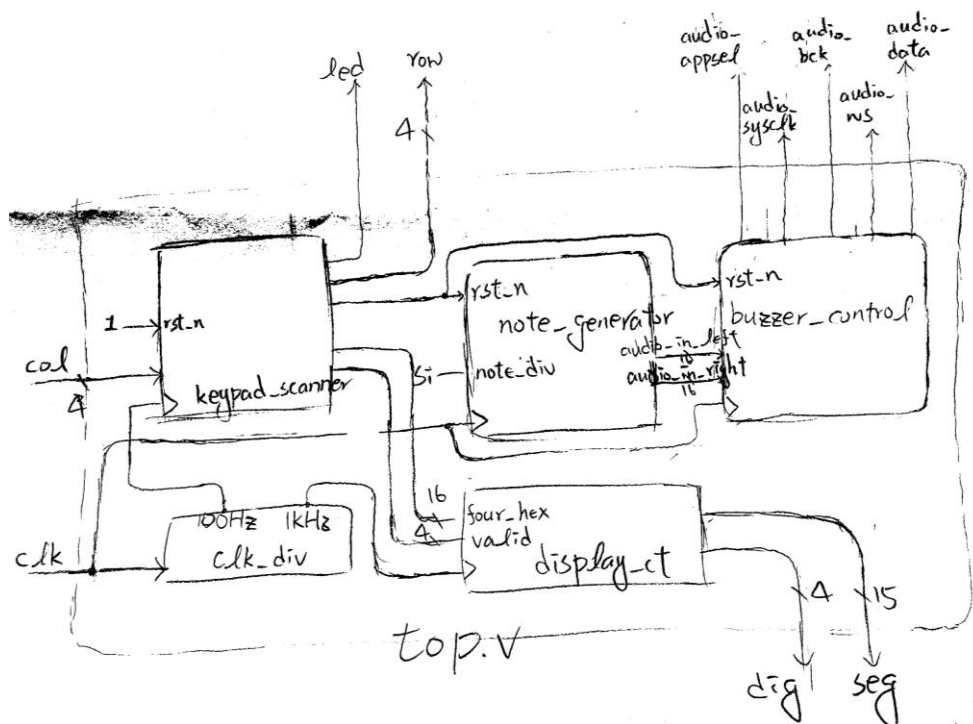- Draw a block diagram for the complete design by re-using existing modules introduced in the class previously and defining any new module.



3. Prepare a UCF file for the input/output pin assignment.

```
1. # output pins association
2. NET "seg[0]" LOC = P6;
3. NET "seg[1]" LOC = N4;
4. NET "seg[2]" LOC = V5;
5. NET "seg[3]" LOC = T5;
6. NET "seg[4]" LOC = U7;
7. NET "seg[5]" LOC = R3;
8. NET "seg[6]" LOC = N5;
9. NET "seg[7]" LOC = R5;
10. NET "seg[8]" LOC = T3;
11. NET "seg[9]" LOC = T4;
12. NET "seg[10]" LOC = V4;
13. NET "seg[11]" LOC = V7;
14. NET "seg[12]" LOC = R7;
15. NET "seg[13]" LOC = T7;
16. NET "seg[14]" LOC = U5 ;
17. NET "dig[0]" LOC = T6;
18. NET "dig[1]" LOC = V6;
19. NET "dig[2]" LOC = U8;
20. NET "dig[3]" LOC = V8;
21. NET "audio_appsel" LOC = H18;
22. NET "audio_sysclk" LOC = H17;
23. NET "audio_bck" LOC = K16;
24. NET "audio_ws" LOC = L15;
25. NET "audio_data" LOC = L16;
26. NET "led" LOC = H5;
27.
28. # input pins association
29. NET "clk" LOC = R10;
30. #NET "dip[0]" LOC = T1;
31. #NET "dip[1]" LOC = P2;
32. #NET "push[0]" LOC = N3;
33. #NET "push[1]" LOC = P4;
34. NET "row[0]" LOC = L3;
35. NET "row[1]" LOC = L4;
36. NET "row[2]" LOC = K1;
37. NET "row[3]" LOC = K2;
38. NET "col[0]" LOC = H1;
39. NET "col[1]" LOC = H2;
```

```
40. NET "col[2]" LOC = J1;
```

```
41. NET "col[3]" LOC = J3;
```

- discussion of any issue or problem worthy of note (yes, even mistakes that you made)

這次遇到的問題是，一開始想要特別寫一個 module 來控制所有東西，所以寫在 keypad\_scanner module 的後面，但是這樣就必須記住前一個狀態的 valid 和 four\_hex 狀態，甚至在 buzzer 響起時，避免使用者繼續輸入密碼做嘗試，還要另外接出一條控制線，所以後來決定直接寫在 scanner 裡面，而且助教已經把各個 state 分好，只要把判斷寫進去就行了。

- optional: any extra feature you added or any suggestion

這次的 bonus 要讓這個密碼鎖可以更改密碼，雖然感覺很簡單，但是實際進去改 keypad scanner 會發現很多地方都需要修改，因此在 lab demo 結束之後才做功能的新增。